

361

Computer Architecture


Lecture 9: Designing Single Cycle Control

361 control.1

Recap: The MIPS Subset


° **ADD and subtract**

- add rd, rs, rt
- sub rd, rs, rt

 

° **OR Imm:**

- ori rt, rs, imm16

 

° **LOAD and STORE**


- lw rt, rs, imm16
- sw rt, rs, imm16

° **BRANCH:**

- beq rs, rt, imm16

° **JUMP:**


- j target

 

361 control.2


Recap: A Single Cycle Datapath

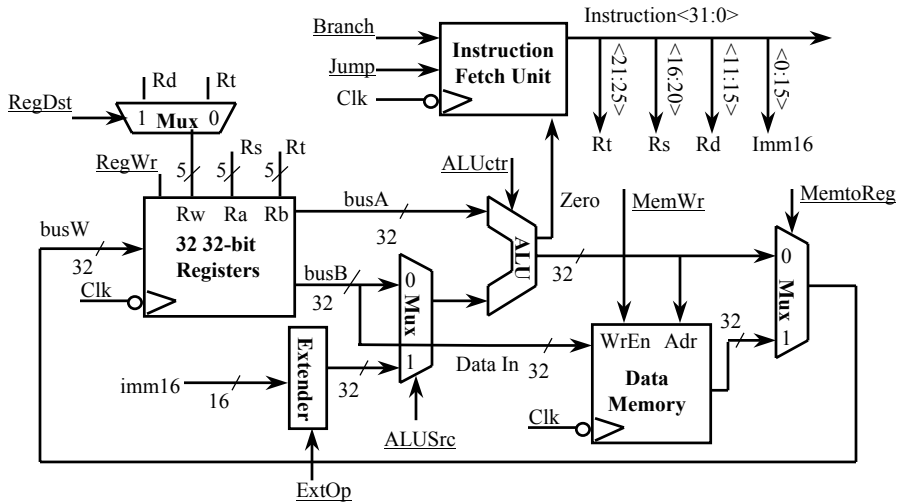- We have everything except control signals (underline)
 - Today's lecture will show you how to generate the control signals



The Big Picture: Where are We Now?

 - The Five Classic Components of a Computer




- Today's Topic: Designing the Control for the Single Cycle Datapath

Outline of Today's Lecture

- Recap and Introduction
- Control for Register-Register & Or Immediate instructions
- Control signals for Load, Store, Branch, & Jump
- Building a local controller: ALU Control
- The main controller
- Summary

361 control.5

RTL: The ADD Instruction

 


◦ **add rd, rs, rt**

- **mem[PC]** **Fetch the instruction from memory**
- **$R[rd] \leftarrow R[rs] + R[rt]$** **The actual operation**
- **$PC \leftarrow PC + 4$** **Calculate the next instruction's address**

361 control.6


Instruction Fetch Unit at the Beginning of Add / Subtract

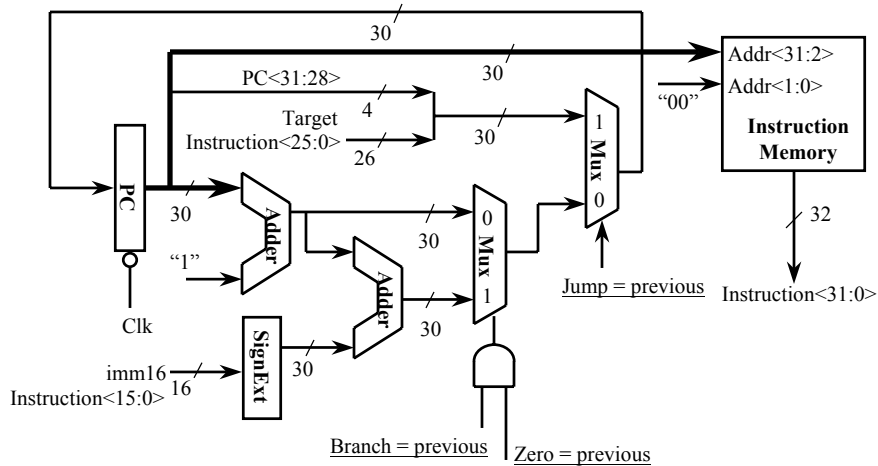- Fetch the instruction from Instruction memory: $\text{Instruction} \leftarrow \text{mem}[\text{PC}]$
 - This is the same for all instructions




361 control.7

 The Single Cycle Datapath during Add and Subtract



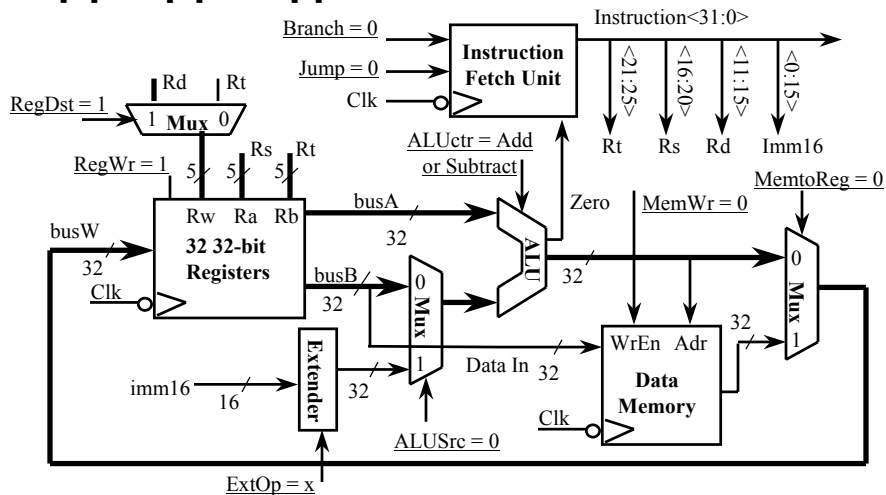- $R[\text{rd}] \leftarrow R[\text{rs}] \text{ +/- } R[\text{rt}]$




361 control.8

Instruction Fetch Unit at the End of Add and Subtract


° $PC \leftarrow PC + 4$

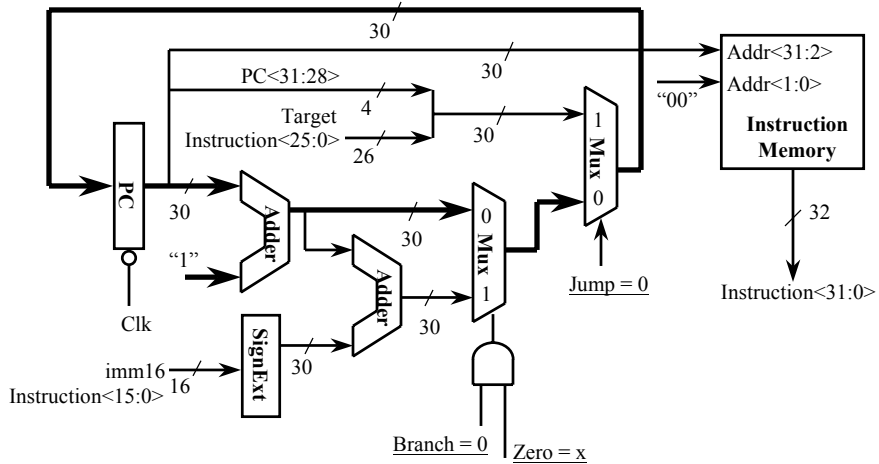- This is the same for all instructions except: Branch and Jump




361 control.9

 The Single Cycle Datapath during Or Immediate




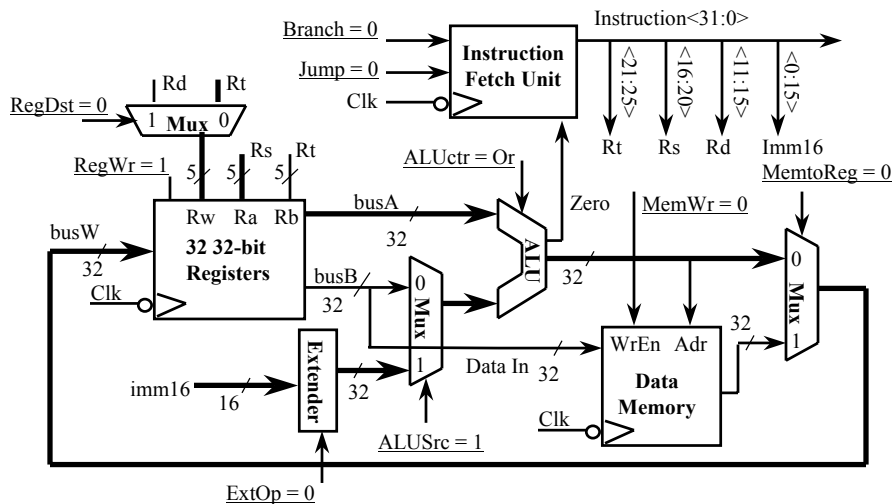° $R[rt] \leftarrow R[rs] \text{ or } \text{ZeroExt}[Imm16]$




361 control.10

The Single Cycle Datapath during Load

 


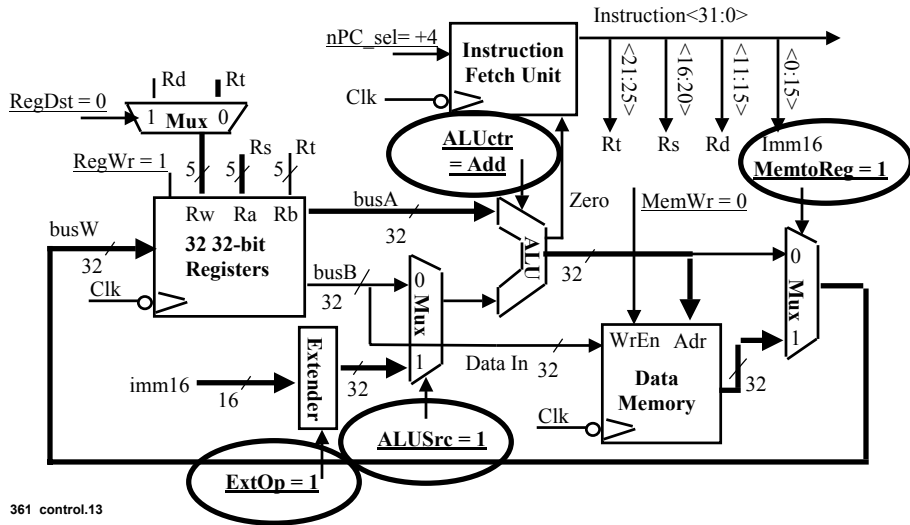◦ $R[rt] \leftarrow \text{Data Memory} \{R[rs] + \text{SignExt}[\text{imm16}]\}$




361 control.13

The Single Cycle Datapath during Store

 


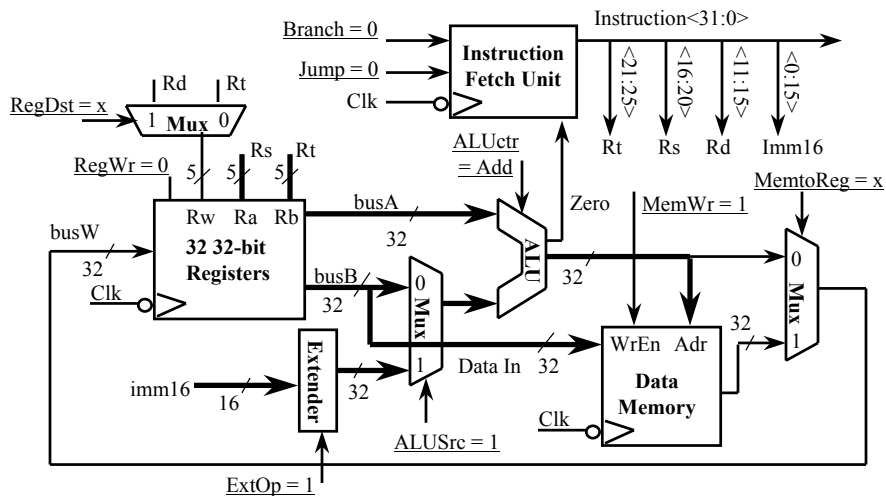◦ $\text{Data Memory} \{R[rs] + \text{SignExt}[\text{imm16}]\} \leftarrow R[rt]$




361 control.14

The Single Cycle Datapath during Store

 


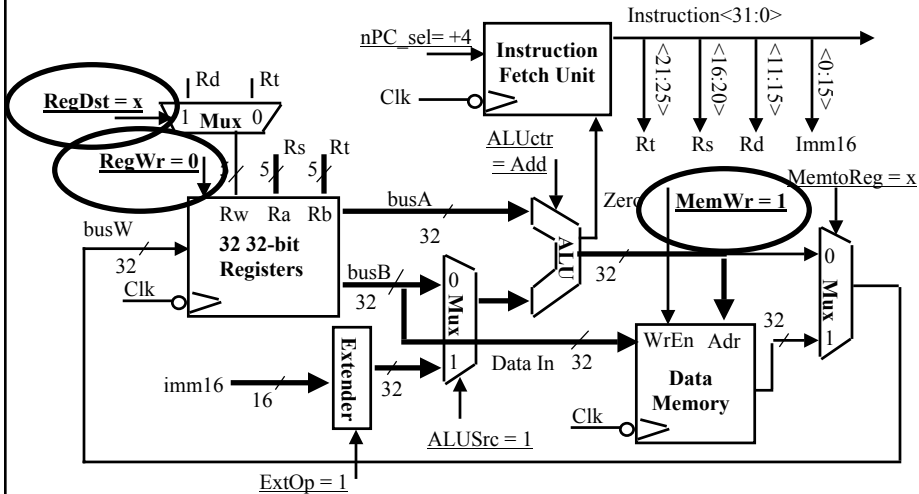° Data Memory {R[rs] + SignExt[imm16]} ← R[rt]




361 control.15

The Single Cycle Datapath during Branch

 


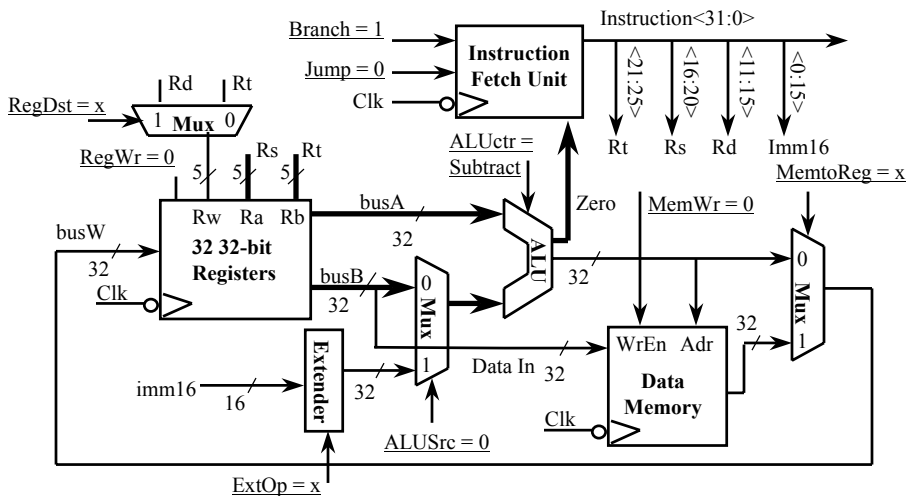° if (R[rs] - R[rt] == 0) then Zero ← 1 ; else Zero ← 0




361 control.16

 Instruction Fetch Unit at the End of Branch




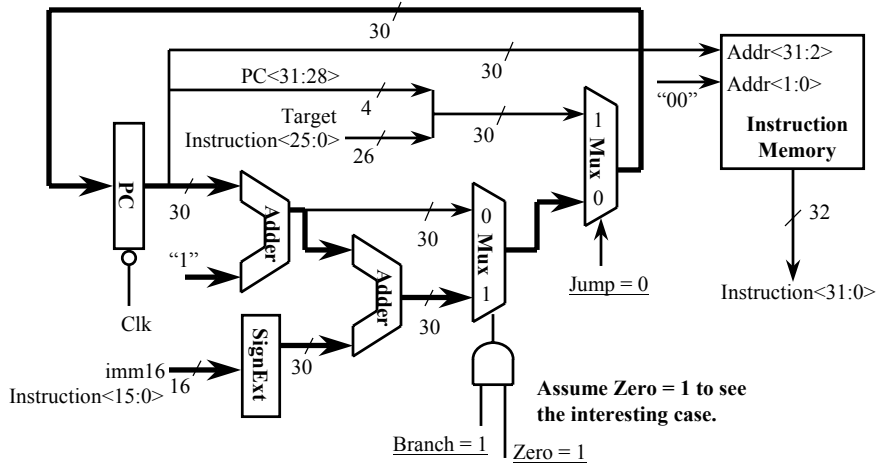° if (Zero == 1) then $PC = PC + 4 + \text{SignExt}[\text{imm16}] * 4$; else $PC = PC + 4$




361 control.17

 Instruction Fetch Unit at the End of Branch




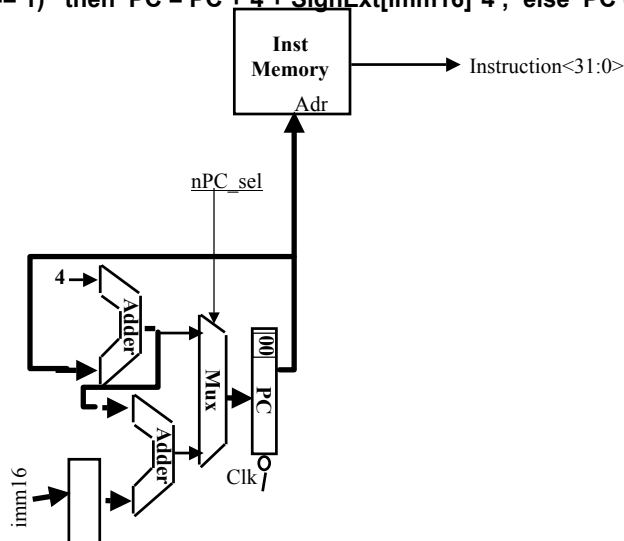° if (Zero == 1) then $PC = PC + 4 + \text{SignExt}[\text{imm16}] * 4$; else $PC = PC + 4$




361 control.18

The Single Cycle Datapath during Jump

 


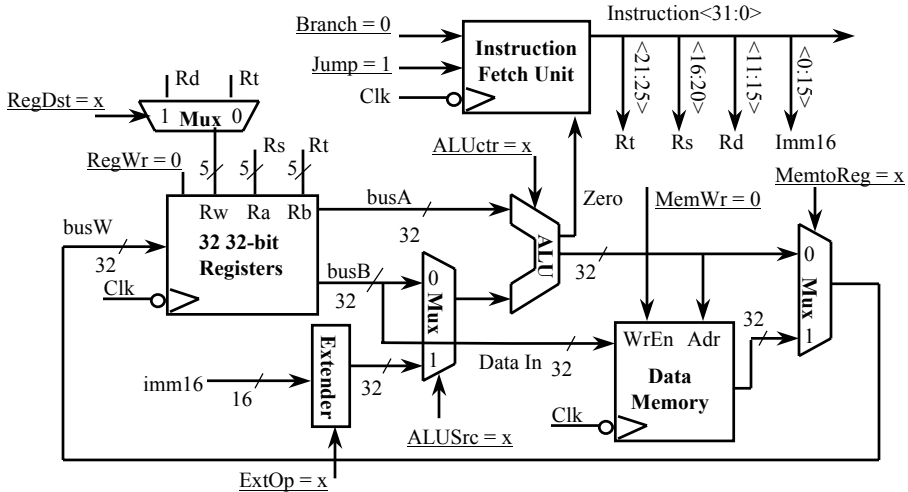- Nothing to do! Make sure control signals are set correctly!




361 control.19

 Instruction Fetch Unit at the End of Jump




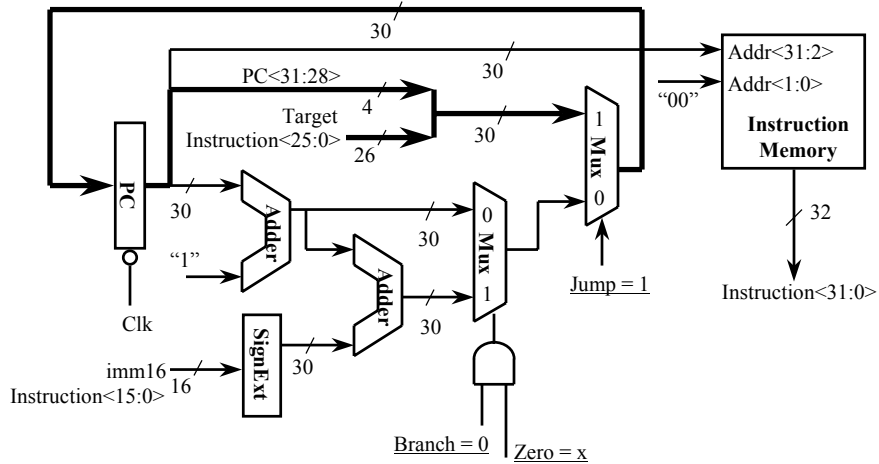- PC <- PC<31:29> concat target<25:0> concat "00"



361 control.20

Step 4: Given Datapath: RTL -> Control

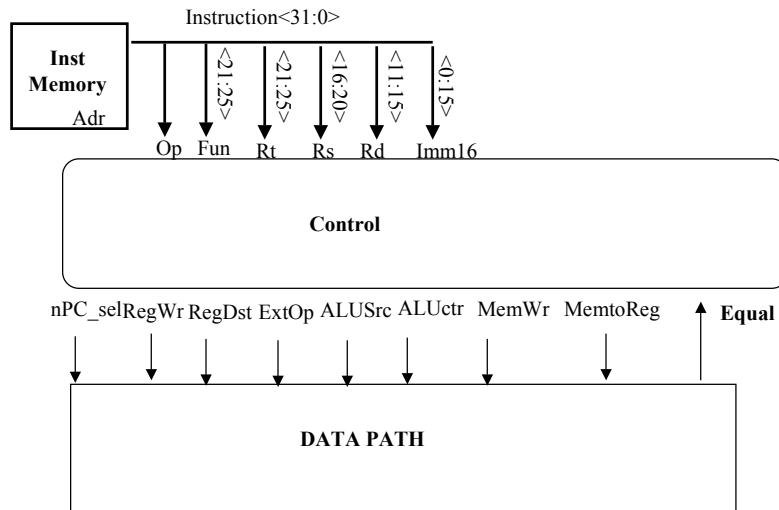

361 control.21

A Summary of Control Signals

inst Register Transfer


ADD	$R[rd] \leftarrow R[rs] + R[rt];$	$PC \leftarrow PC + 4$
	$ALUSrc = \text{RegB}, ALUctr = \text{"add"}, \text{RegDst} = rd, \text{RegWr}, nPC_sel = \text{"+4"}$	
SUB	$R[rd] \leftarrow R[rs] - R[rt];$	$PC \leftarrow PC + 4$
	$ALUSrc = \text{RegB}, ALUctr = \text{"sub"}, \text{RegDst} = rd, \text{RegWr}, nPC_sel = \text{"+4"}$	
Ori	$R[rt] \leftarrow R[rs] + \text{zero_ext}(\text{Imm16});$	$PC \leftarrow PC + 4$
	$ALUSrc = \text{Im}, \text{Extop} = \text{"Z"}, ALUctr = \text{"or"}, \text{RegDst} = rt, \text{RegWr}, nPC_sel = \text{"+4"}$	
LOAD	$R[rt] \leftarrow \text{MEM}[R[rs] + \text{sign_ext}(\text{Imm16})];$	$PC \leftarrow PC + 4$
	$ALUSrc = \text{Im}, \text{Extop} = \text{"Sn"}, ALUctr = \text{"add"},$ $\text{MemtoReg}, \text{RegDst} = rt, \text{RegWr}, \quad nPC_sel = \text{"+4"}$	
STORE	$\text{MEM}[R[rs] + \text{sign_ext}(\text{Imm16})] \leftarrow R[rs];$	$PC \leftarrow PC + 4$
	$ALUSrc = \text{Im}, \text{Extop} = \text{"Sn"}, ALUctr = \text{"add"}, \text{MemWr}, nPC_sel = \text{"+4"}$	
BEQ	if ($R[rs] == R[rt]$) then $PC \leftarrow PC + \text{sign_ext}(\text{Imm16})$ 00 else $PC \leftarrow PC + 4$	
	$nPC_sel = \text{"Br"}, ALUctr = \text{"sub"}$	

361 control.22

A Summary of the Control Signals

See Appendix A → func
Appendix A → op


	10 0000	10 0010	We Don't Care :-)				
	00 0000	00 0000	00 1101	10 0011	10 1011	00 0100	00 0010
	add	sub	ori	lw	sw	beq	jump
RegDst	1	0	0	0	x	x	x
ALUSrc	0	0	1	1	1	0	x
MemtoReg	0	0	0	1	x	x	x
RegWrite	1	1	1	1	0	0	0
MemWrite	0	0	0	0	1	0	0
Branch	0	0	0	0	0	1	0
Jump	0	0	0	0	0	0	1
ExtOp	x	x	0	1	1	x	x
ALUctr<2:0>	Add	Subtract	Or	Add	Add	Subtract	xxx

 

361 control.23


The Concept of Local Decoding

op	00 0000	00 1101	10 0011	10 1011	00 0100	00 0010
	R-type	ori	lw	sw	beq	jump
RegDst	1	0	0	x	x	x
ALUSrc	0	1	1	1	0	x
MemtoReg	0	0	1	x	x	x
RegWrite	1	1	1	0	0	0
MemWrite	0	0	0	1	0	0
Branch	0	0	0	0	1	0
Jump	0	0	0	0	0	1
ExtOp	x	0	1	1	x	x
ALUop<N:0>	"R-type"	Or	Add	Add	Subtract	xxx

 

361 control.24

The Encoding of ALUop

 


- In this exercise, ALUop has to be 2 bits wide to represent:
 - (1) “R-type” instructions
 - “I-type” instructions that require the ALU to perform:
 - (2) Or, (3) Add, and (4) Subtract
- To implement the full MIPS ISA, ALUop has to be 3 bits to represent:
 - (1) “R-type” instructions
 - “I-type” instructions that require the ALU to perform:
 - (2) Or, (3) Add, (4) Subtract, and (5) And (Example: andi)


	R-type	ori	lw	sw	beq	jump
ALUop (Symbolic)	“R-type”	Or	Add	Add	Subtract	xxx
ALUop<2:0>	1 00	0 10	0 00	0 00	0 01	xxx

361 control.25

The Decoding of the “func” Field

 

	R-type	ori	lw	sw	beq	jump
ALUop (Symbolic)	“R-type”	Or	Add	Add	Subtract	xxx
ALUop<2:0>	1 00	0 10	0 00	0 00	0 01	xxx

 

(P. 286 text)

func<5:0>	Instruction Operation
10 0000	add
10 0010	subtract
10 0100	and
10 0101	or
10 1010	set-on-less-than



ALUctr<2:0>	ALU Operation
000	Add
001	Subtract
010	And
110	Or
111	Set-on-less-than

361 control.26

The Truth Table for ALUctr

ALUop (Symbolic)	R-type	ori	lw	sw	beq
	"R-type"	Or	Add	Add	Subtract
ALUop<2:0>	1 00	0 10	0 00	0 00	0 01

func<3:0>	Instruction Op.
0000	add
0010	subtract
0100	and
0101	or
1010	set-on-less-than

ALUop			func				ALU	ALUctr		
bit<2>	bit<1>	bit<0>	bit<3>	bit<2>	bit<1>	bit<0>	Operation	bit<2>	bit<1>	bit<0>
0	0	0	x	x	x	x	Add	0	1	0
0	x	1	x	x	x	x	Subtract	1	1	0
0	1	x	x	x	x	x	Or	0	0	1
1	x	x	0	0	0	0	Add	0	1	0
1	x	x	0	0	1	0	Subtract	1	1	0
1	x	x	0	1	0	0	And	0	0	0
1	x	x	0	1	0	1	Or	0	0	1
1	x	x	1	0	1	0	Set on <	1	1	1

361 control.27

The Logic Equation for ALUctr<2>

ALUop			func				ALUctr<2>
bit<2>	bit<1>	bit<0>	bit<3>	bit<2>	bit<1>	bit<0>	
0	x	1	x	x	x	x	1
1	x	x	0	0	1	0	1
1	x	x	1	0	1	0	1

X Y Z A B C D

This makes func<3> a don't care

$$\circ \text{ALUctr<2>} = \text{!ALUop<2>} \& \text{ALUop<0>} + \text{ALUop<2>} \& \text{!func<2>} \& \text{func<1>} \& \text{!func<0>}$$

$$= \text{!X\&Y} + \text{X\&!A\&!B\&C\&!D} + \text{X\&A\&!B\&C\&!D}$$

$$= \text{!X\&Y} + \text{X\&!B\&C\&!D}$$

361 control.28

The Logic Equation for ALUctr<1>

ALUop			func				ALUctr<1>
bit<2>	bit<1>	bit<0>	bit<3>	bit<2>	bit<1>	bit<0>	
0	0	0	x	x	x	x	1
0	x	1	x	x	x	x	1
1	x	x	0	0	0	0	1
1	x	x	0	0	1	0	1
1	x	x	1	0	1	0	1

$$\circ \text{ALUctr<1>} = \text{!ALUop<2>} \& \text{!ALUop<0>} + \text{ALUop<2>} \& \text{!func<2>} \& \text{!func<0>}$$

361 control.29


The Logic Equation for ALUctr<0>

ALUop			func				ALUctr<0>
bit<2>	bit<1>	bit<0>	bit<3>	bit<2>	bit<1>	bit<0>	
0	1	x	x	x	x	x	1
1	x	x	0	1	0	1	1
1	x	x	1	0	1	0	1

$$\circ \text{ALUctr<0>} = \text{!ALUop<2>} \& \text{ALUop<0>} + \text{ALUop<2>} \& \text{!func<3>} \& \text{func<2>} \& \text{!func<1>} \& \text{func<0>} + \text{ALUop<2>} \& \text{func<3>} \& \text{!func<2>} \& \text{func<1>} \& \text{!func<0>}$$

361 control.30

The ALU Control Block

 

- $ALUctr<2> = !ALUop<2> \& ALUop<0> +$
 $ALUop<2> \& !func<2> \& func<1> \& !func<0>$
- $ALUctr<1> = !ALUop<2> \& !ALUop<0> +$
 $ALUop<2> \& !func<2> \& !func<0>$
- $ALUctr<0> = !ALUop<2> \& ALUop<0>$
 $+ ALUop<2> \& !func<3> \& func<2> \& !func<1> \& func<0>$
 $+ ALUop<2> \& func<3> \& !func<2> \& func<1> \& !func<0>$

361 control.31

Step 5: Logic for each control signal

- $nPC_sel \leq \text{if } (OP == BEQ) \text{ then } EQUAL \text{ else } 0$
- $ALUsrc \leq \text{if } (OP == \text{"Rtype"}) \text{ then "regB" else "immed"}$
- $ALUctr \leq \text{if } (OP == \text{"Rtype"}) \text{ then } funct$
 $\text{elseif } (OP == \text{"ORi"}) \text{ then "OR"}$
 $\text{elseif } (OP == \text{"BEQ"}) \text{ then "sub"}$
 else "add"
- $ExtOp \leq \underline{\hspace{2cm}}$
- $MemWr \leq \underline{\hspace{2cm}}$
- $MemtoReg \leq \underline{\hspace{2cm}}$
- $RegWr: \leq \underline{\hspace{2cm}}$
- $RegDst: \leq \underline{\hspace{2cm}}$


361 control.32

Step 5: Logic for each control signal

- **nPC_sel** <= if (OP == BEQ) then EQUAL else 0
- **ALUSrc** <= if (OP == "Rtype") then "regB" else "immed"
- **ALUctr** <= if (OP == "Rtype") then funct
 elseif (OP == ORi) then "OR"
 elseif (OP == BEQ) then "sub"
 else "add"
- **ExtOp** <= if (OP == ORi) then "zero" else "sign"
- **MemWr** <= (OP == Store)
- **MemtoReg** <= (OP == Load)
- **RegWr:** <= if ((OP == Store) || (OP == BEQ)) then 0 else 1
- **RegDst:** <= if ((OP == Load) || (OP == ORi)) then 0 else 1

361 control.33

The "Truth Table" for the Main Control

 

op	00 0000	00 1101	10 0011	10 1011	00 0100	00 0010
	R-type	ori	lw	sw	beq	jump
RegDst	1	0	0	x	x	x
ALUSrc	0	1	1	1	0	x
MemtoReg	0	0	1	x	x	x
RegWrite	<u>1</u>	<u>1</u>	<u>1</u>	<u>0</u>	<u>0</u>	<u>0</u>
MemWrite	0	0	0	1	0	0
Branch	0	0	0	0	1	0
Jump	0	0	0	0	0	1
ExtOp	x	0	1	1	x	x
ALUop (Symbolic)	"R-type"	Or	Add	Add	Subtract	xxx
ALUop <2>	1	0	0	0	0	x
ALUop <1>	0	1	0	0	0	x
ALUop <0>	0	0	0	0	1	x

361 control.34

The "Truth Table" for RegWrite


op	00 0000	00 1101	10 0011	10 1011	00 0100	00 0010
	R-type	ori	lw	sw	beq	jump
RegWrite	1	1	1	x	x	x

° RegWrite = R-type + ori + lw

= !op<5> & !op<4> & !op<3> & !op<2> & !op<1> & !op<0> (R-type)


+ !op<5> & !op<4> & op<3> & op<2> & !op<1> & op<0> (ori)

 + op<5> & !op<4> & !op<3> & !op<2> & op<1> & op<0> (lw)




361 control.35

PLA Implementation of the Main Control

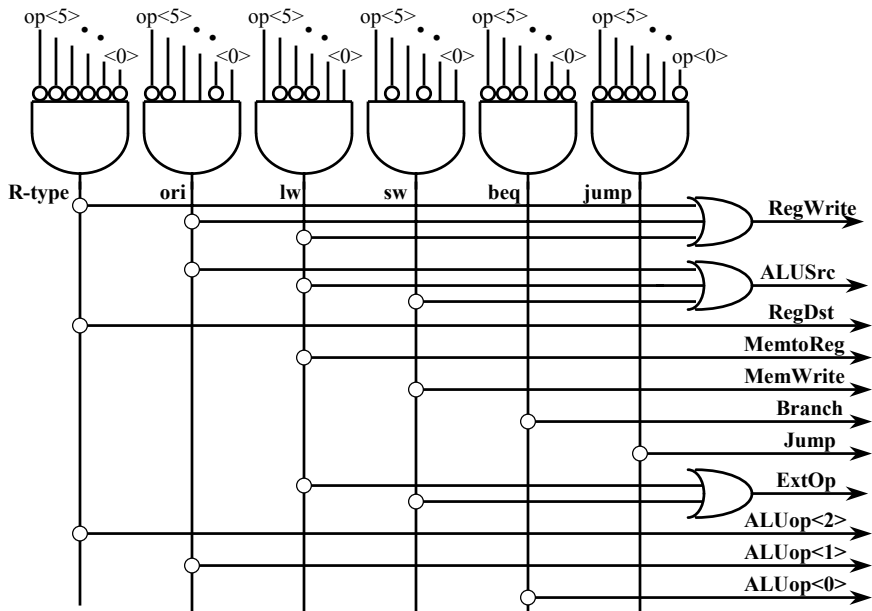


361 control.36

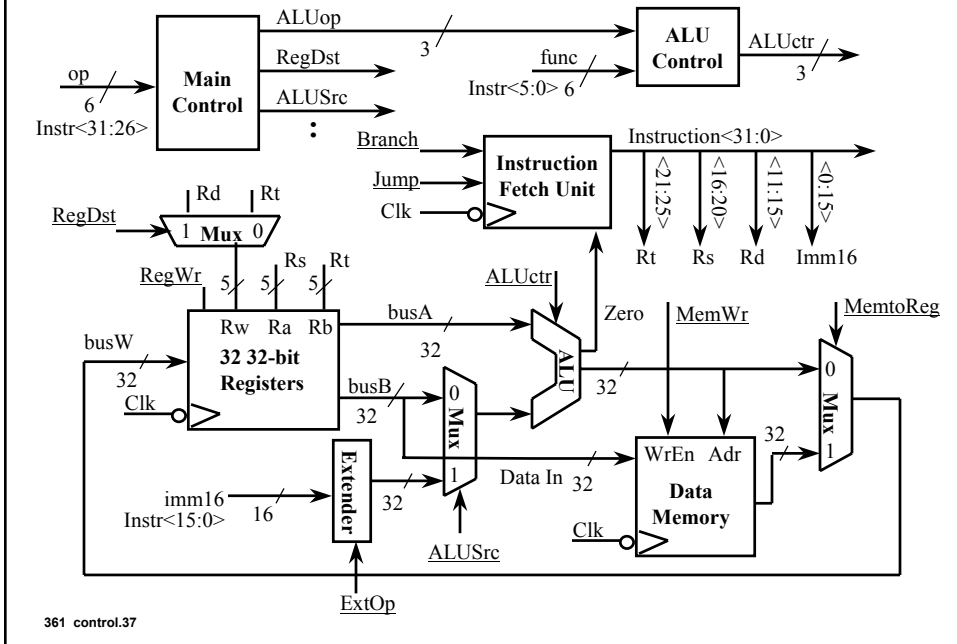Putting it All Together: A Single Cycle Processor




Clocking Methodology

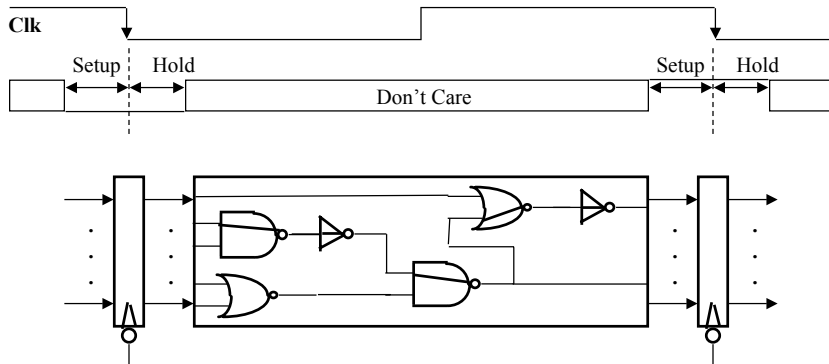

- All storage elements are clocked by the same clock edge
- Cycle Time = CLK-to-Q + Longest Delay Path + Setup + Clock Skew
- (CLK-to-Q + Shortest Delay Path - Clock Skew) > Hold Time

Worst Case Timing (Load)

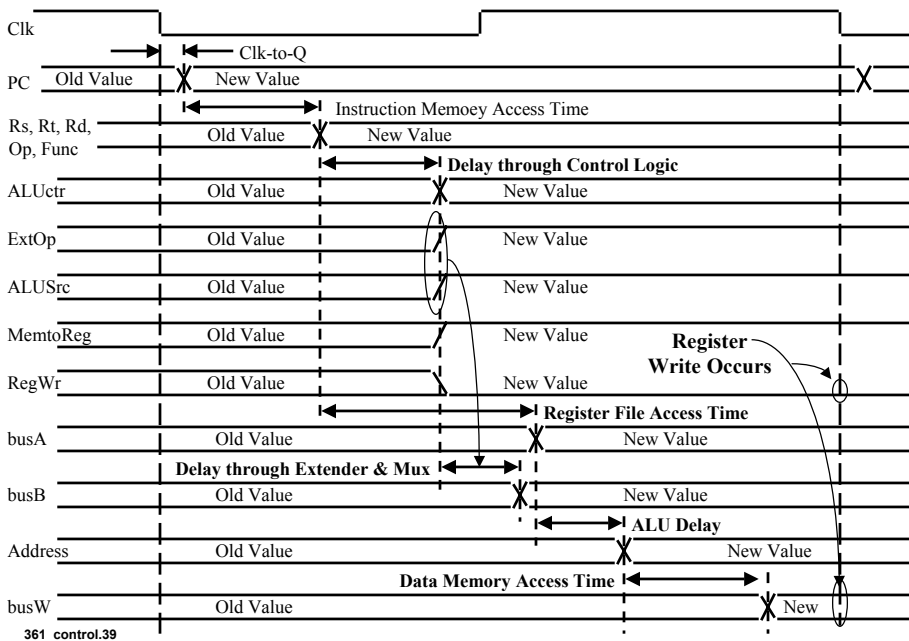

Drawback of this Single Cycle Processor

- Long cycle time:
 - Cycle time must be long enough for the load instruction:
 - PC's Clock -to-Q +
 - Instruction Memory Access Time +
 - Register File Access Time +
 - ALU Delay (address calculation) +
 - Data Memory Access Time +
 - Register File Setup Time +
 - Clock Skew
- Cycle time is much longer than needed for all other instructions

Summary

- Single cycle datapath => CPI=1, CCT => long
- 5 steps to design a processor
 - 1. Analyze instruction set => datapath requirements
 - 2. Select set of datapath components & establish clock methodology
 - 3. Assemble datapath meeting the requirements
 - 4. Analyze implementation of each instruction to determine setting of control points that effects the register transfer.
 - 5. Assemble the control logic
- Control is the hard part
- MIPS makes control easier
 - Instructions same size
 - Source registers always in same place
 - Immediates same size, location
 - Operations always on registers/immediates

